

Introduction to HVDC

LCC & VSC - Comparison

Dr Radnya A Mukhedkar

*Group Leader, Senior Principal Engineer
System Design*

ALSTOM

HVDC Converter Technology


1. Line Commutate Converter (LCC) HVDC

- Current Sourced Converter
- Thyristor based Technology

2. Voltage Sourced Converter (VSC)

- Self Commutated Converter
- Transistor (IGBT, GTO etc.) based Technology


LCC – HVDC Scheme

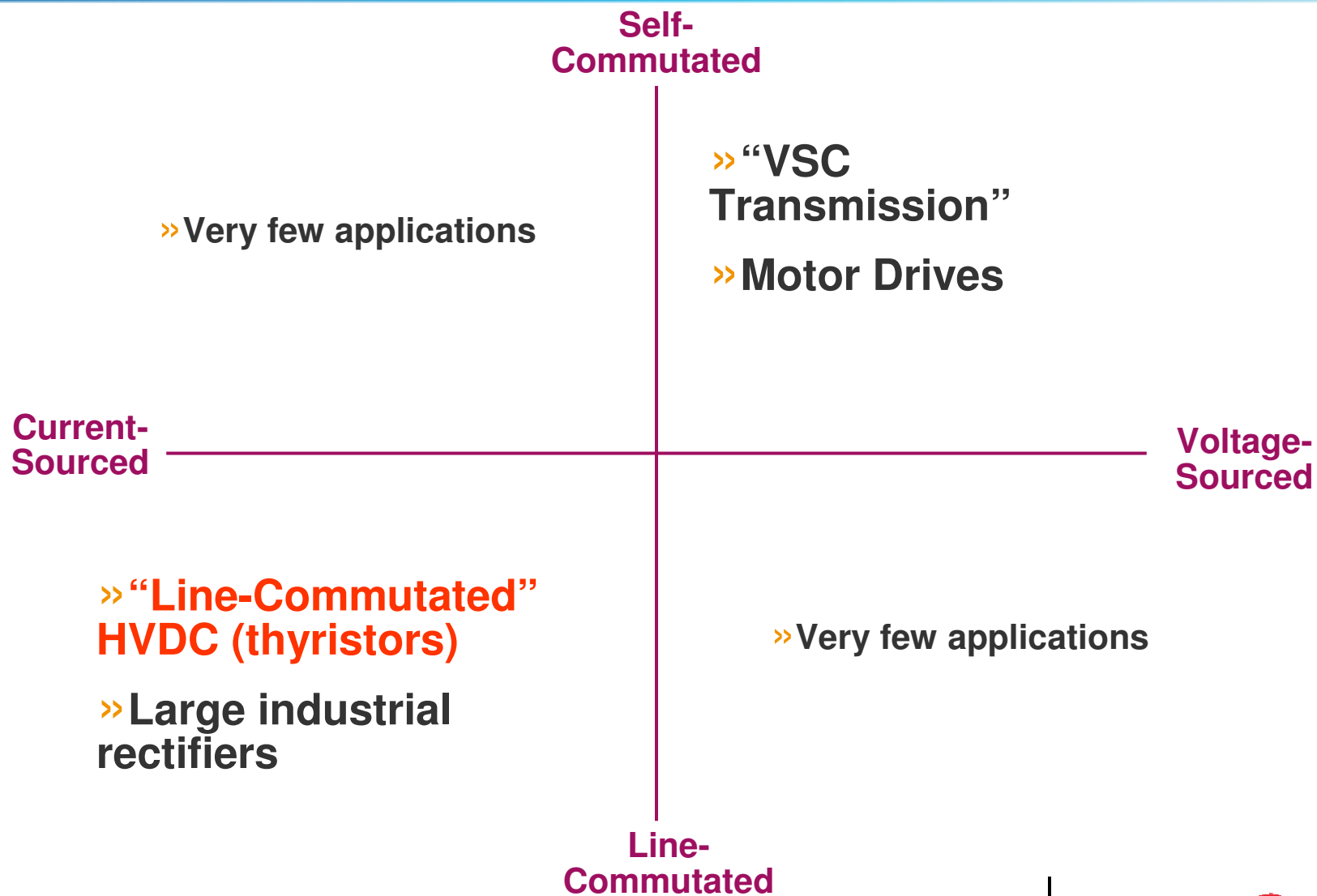

VSC vs LCC HVDC


LCC HVDC

- Current-sourced
- Line-Commutated

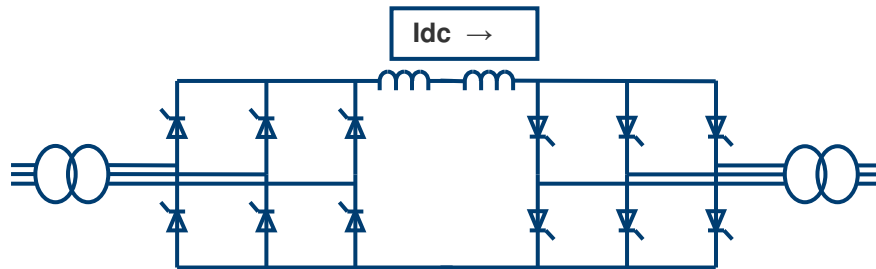

VSC HVDC

- Voltage-Sourced
- Self-Commutated

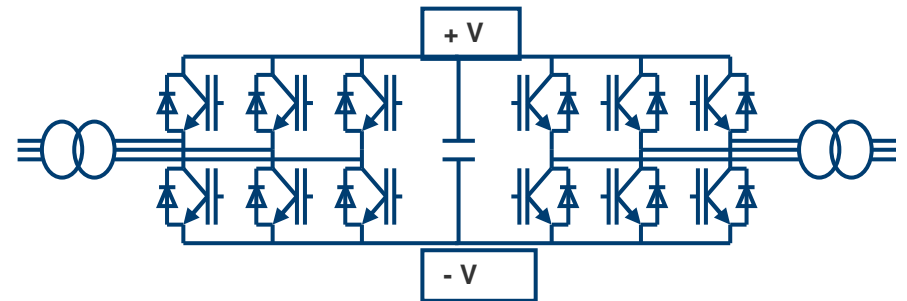

Voltage-Sourced versus Current-Sourced converters


LCC HVDC

- Use semiconductors which can withstand voltage in either polarity
- Output voltage can be either polarity to change power direction
- Current direction does not change
- Store energy inductively
- Use semiconductors which can turn on by control action
- Turn-off and “commutation” rely on the external circuit

VSC HVDC

- Use semiconductors which can pass current in either direction
- Output voltage polarity does not change
- Current direction changes to change Power direction
- Store energy capacitively
- Use semiconductors which can turn on or off by control action
- Turn-off is independent of external circuit

Converter Rating

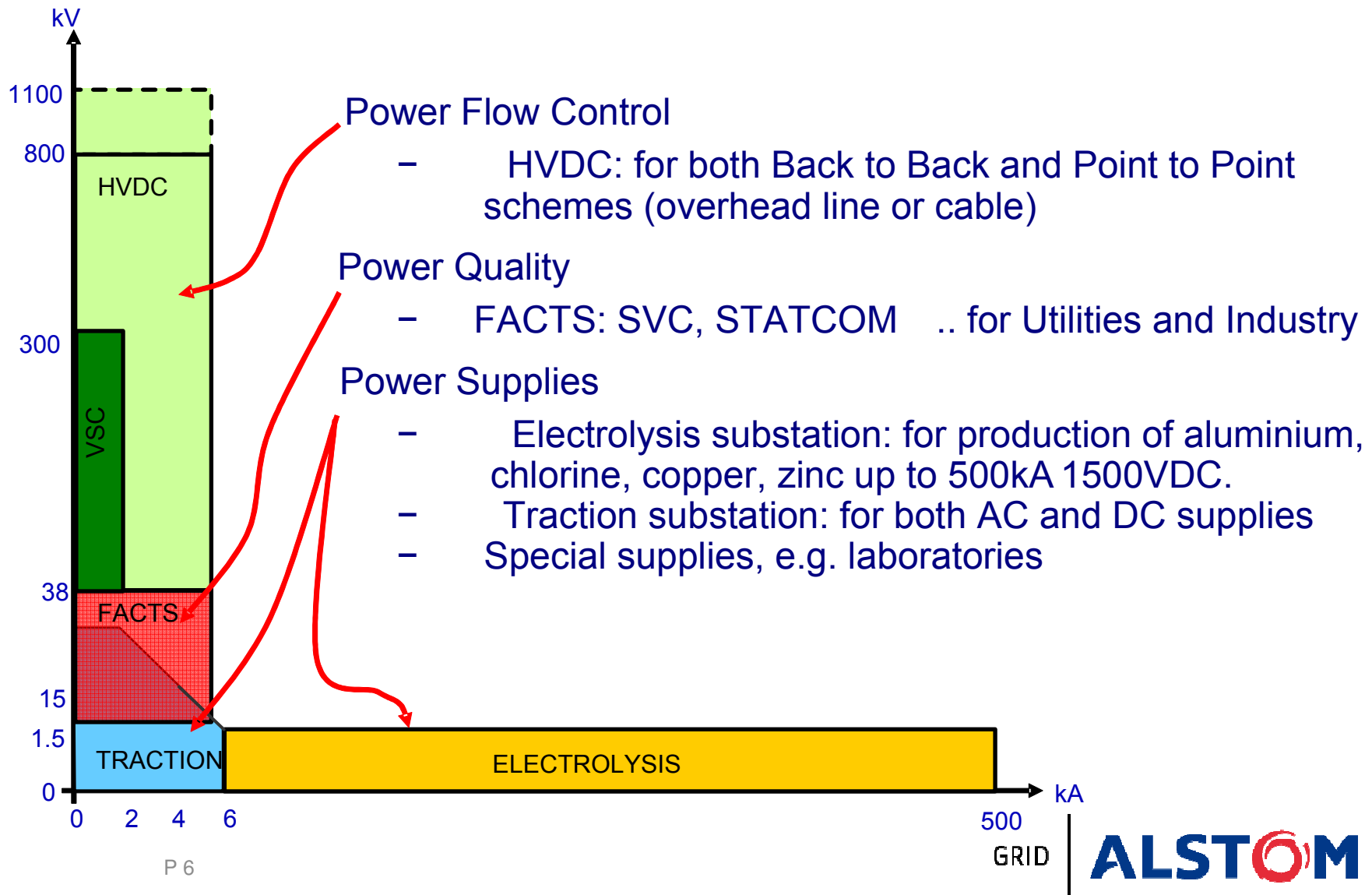

LCC vs VSC Comparison

LCC HVDC

- High power capability,
 - PE device current capability
- Good overload capability
- Requires stronger AC systems
- “Black” start capability, requires additional equipment
- Generates harmonic distortion, AC & DC harmonic filters required
- Coarser reactive power control
- Large site area, dominated by harmonic filters

VSC HVDC

- Lower power capability
 - PE device current capability
- Weak overload capability
- Operates into weaker AC systems
- “Black” start capability
- Insignificant level of harmonic generation, hence no filters required
- Finer reactive power control
- Compact site area, 50 – 60% of LCC site area

LCC vs VSC Comparison

LCC HVDC

- Requires converter transformers
 - continuous DC Voltage stress
- Lower station losses
- Lower cost
- Higher reliability
- More mature technology
- Power is reversed by changing polarity of the converters
- Requires use of MI cables
 - Higher voltage capability

VSC HVDC

- Use of conventional transformers
 - Symmetrical monopole
- Higher station losses
- Higher cost by 10 – 15%
- Lower reliability, due to high component count
- Less mature technology
- Power is reversed by changing direction of current flow
- Ideal for use with XLPE cables
 - Lower voltage capability

www.alstom.com

ALSTOM